

EE 201.3 (Sections 01/03)
(Instructors: Dr. Daniel Teng/Denard Lynch)

Final Examination

Friday, December 9, 2005

9:00 AM

Time Allowed: 3 Hours

**Materials allowed: One 8½" X 11" sheet of notes,
Calculators**

Instructions:

- Answer all questions in the space provided (use page backs for rough work if necessary)
- State your assumptions; show all relevant work. Box, circle or otherwise highlight your answers. Please try to write neatly.
- Put your name and student number on the cover page; put *only* your student number on all remaining pages.
- Weighting for each question is indicated in the left margin (Total marks:)

2	3	4	5	6	7	Total
/	/	/	/	/	/	/

Name: _____

Student Number: _____

1) Energy is stored in inductors in the form of:

[1]

- i) Current ii) Magnetic field iii) Voltage iv) Charges

2) Energy is stored in capacitors in the form of:

[1]

- i) Current ii) Magnetic field iii) Voltage iv) Charges


3) Convert $v = 15\sin(120\pi t + 20^\circ)$ to phasor form.

[2]

4) Determine the direction of the induced current in the rectangular loop *when it falls into* a magnetic field \mathbf{B} as shown in the figure on the right.

[2]

- i) Clockwise ii) Counterclockwise

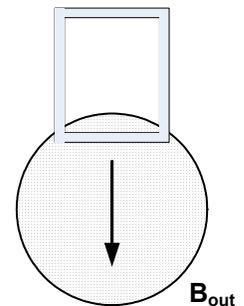

5) The effective value of $v = a + 10\sin(377t + 50^\circ)$ is 8.66. Determine a .

[3]

6) Determine the number of cycles in 0.25 seconds for $\sin(377t + 80^\circ)$.


[2]

7) Determine the number of turns required to make an $8\mu\text{H}$ air core inductor that is 100mm long and has a circular cross-section with radius equal to 5mm.

[3]

8) For the network shown below:
[5]

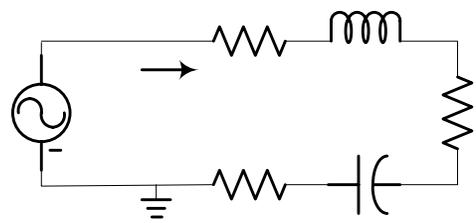a) Determine the frequency, f_{\max} , of the ac voltage source that results in the maximum current, I .




b) Establish and sketch the power triangle for the network at the frequency f_{\max} .

9) A wire conductor carrying a current $I = 50\text{mA}$ is lying in the x - y plane with one end at $(-2\text{cm}, -3\text{cm})$ and the other end at $(10\text{cm}, 6\text{cm})$. Assume the magnetic field $B = 0.5\text{T}$.

Determine the net magnetic force (**magnitude and direction**) exerting on the wire.

[4]

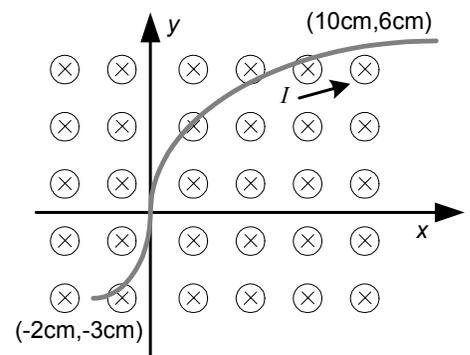

10) A series R - L - C resonant circuit is connected to a source $E = 2\angle 0^\circ$. The total resistance of the circuit is 5Ω . (Assume ideal components)


[5]

a) Determine the reactance, X_L , of the inductor if the quality factor, Q , of the resonant circuit is 25.

b) Determine voltage across inductor.

11) The **current** through an inductor is shown in the graph below. (The numbers on the graph aren't sequential...it looks like a mistake?)


[5]

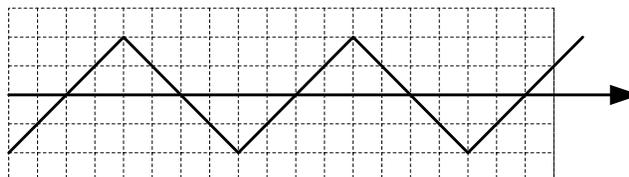


a) Determine the average value of the current.

b) Calculate the effective value of the **voltage** across the inductor if $L = 1\text{mH}$.

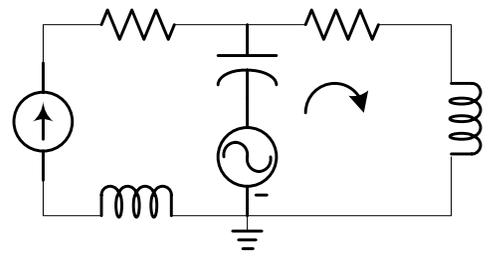
- 12) Determine the current I_L for the following network. [*Hint: Use mesh analysis, but you don't need any matrix math!*]
 [8]



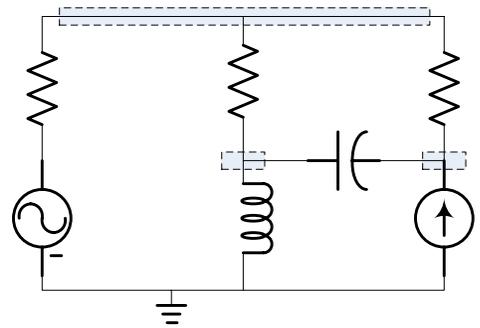
- 13) Write the nodal equations for the following network.
 [8]



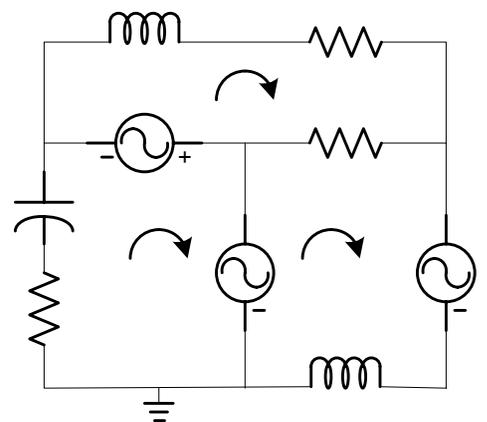- 14) Write the mesh equations for the following network.
 [8]



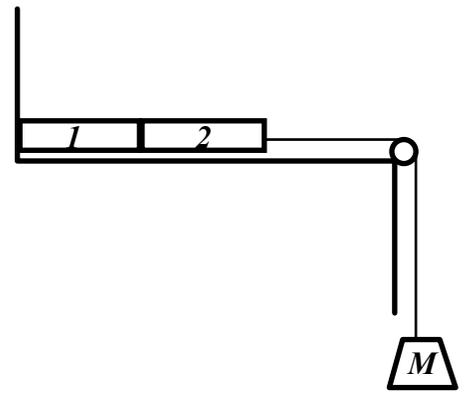- 15) Two permanent magnets are arranged as shown in the sketch. They are both made out of cobalt and are each 2.5cm long with a circular cross-section of $.0008\text{m}^2$. Each has strength of 22.5A-t. One is firmly attached to a wall, and the other is attached through a paramagnetic cable to a mass, M . The two magnets are in contact with each other (i.e. no gap).



[7]

The relative permeability of the cobalt, μ_r , is 800, and can be considered constant over the range of interest. What is the maximum mass that the system can support before the magnets are pulled apart?

[**Hint:** You can consider the reluctance of the path through the air outside the magnets to be zero.]

- 16) The loading of a factory on a 1000V, 60-Hz supply includes:

- 20-kW electric heating (unity power factor)
- 10-kW of induction motors (0.7 lagging power factor)
- 5-kW fluorescent lighting (0.85 lagging power factor)

[7]

- a) Determine the total real power, P , reactive power, Q , and apparent power, S , for the combined load.


- b) Draw the Power Triangle for the combined load.

- c) What is the power factor, F_p for the combined load?

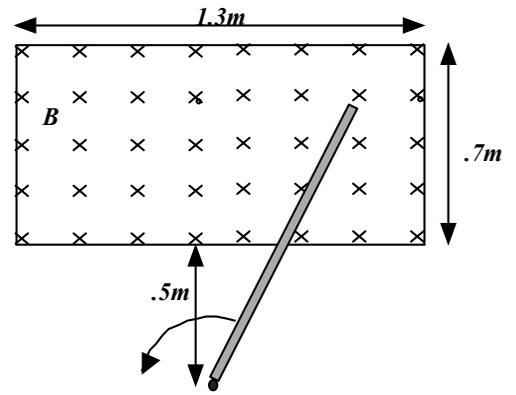- 17) A 1m long rigid wire is rotated at 600rpm through a uniform magnet field of density $B = 0.7T$, which is directed into the page.

[7]


Find the maximum voltage that would be observed between the ends of the wire. (*Hint: recall from your assignments that the incremental voltage, dE , induced in a segment dr is given by $dE = B\omega r dr$*)



- 18) The network shown below is used to deliver power from the 10V source to the load.

[8]

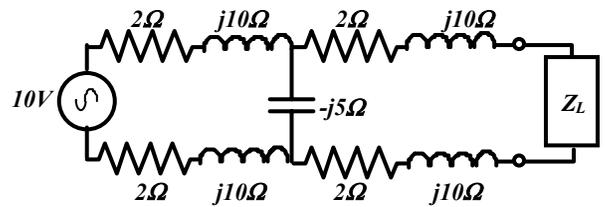- a) What is the Thevenin Equivalent impedance, Z_{Th} , of the supply network (as seen by the load)?




- b) If the load impedance, $Z_L = (R_L - j5)\Omega$, what value of load resistance, R_L , will provide the maximum power transferred to the load?

- 19) For the network shown below, $e = \sin(500t + 20^\circ)$. Assume the switch has been on position 1 for a long time and moved to position 2 at time $t = 0$

[5]

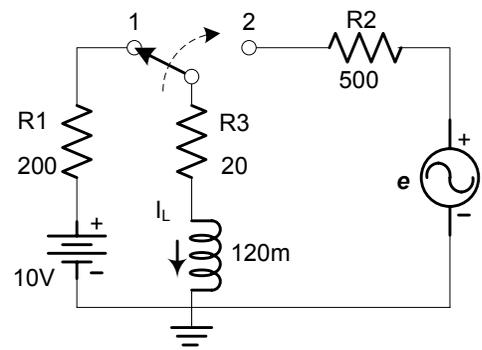- a) Determine the initial current through inductor L at time $t = 0$.



- b) Find the value of the current through the inductor at $t = 2s$.

- 20) A motor can be modeled as $R + jX_L = (13 + jX_L)\Omega$. A capacitor $C = 100\mu F$ is required to raise the power factor to 1 when it is connected to a 60Hz supply.

[9]

- a) Determine X_L of the motor given that the angle, θ , of the motor's impedance is $< 45^\circ$

[Hint: recall that the roots of a quadratic equation are given by $x_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$]

- b) Determine the power factor of the motor *before* the compensation.

Some potentially useful constants/relationships:

Acceleration of gravity: $g = 9.81 \text{ m/s}^2$

Magnetic force of attraction: $F_{att} = \frac{B^2 A}{2\mu_0}$

Permeability of free space: $\mu_0 = 4\pi \times 10^{-7} \text{ Wb/At-m}$

1hp = 746Watts

Magnetic field, B , a distance d from a wire carrying current I : $B = \frac{\mu_0 I}{2\pi d} = \frac{k_m I}{d}$